

7.1 Basic Properties of Boolean Algebra

• Basic Properties of Boolean algebra:

Table 7.1.1: A few basic properties of Boolean algebra.

Property	Name	Description
$a(b + c) = ab + ac$	Distributive (for AND)	Same as multiplication in regular algebra
$a + a' = 1$	Complement	Clearly one of a, a' must be 1 $1 + 0 = 1$ $0 + 1 = 1$
$a \cdot 1 = a$	Identity	Result of $a \cdot 1$ is always a 's value $0 \cdot 1 = 0$ $1 \cdot 1 = 1$

• More Properties!

Table 7.1.2: More properties.

Property	Name	Description
$ab = ba$	Commutative (for AND)	Same as multiplication for regular algebra
$a + b = b + a$	Commutative (for OR)	Same as addition for regular algebra
$a + 1 = 1$	Null elements	OR only needs one 1 to evaluate to 1 $a = 0 \quad 0 + 1 = 1$ $a = 1 \quad 1 + 1 = 1$
$a + a = a$ $aa = a$	Idempotent	$0 + 0 = 0 \quad 1 + 1 = 1$ $0 \cdot 0 = 0 \quad 1 \cdot 1 = 1$

• More Properties!

Table 7.1.3: Commonly used basic properties of Boolean algebra.

Property	Name	Description
$a(b + c) = ab + ac$ $a + (bc) = (a + b)(a + c)$	Distributive (AND) Distributive (OR)	(AND) Same as multiplication in regular algebra (OR) Different from regular algebra
$ab = ba$ $a + b = b + a$	Commutative	Variable order does not matter. Good practice is to sort variables alphabetically.
$(ab)c = a(bc)$ $(a + b) + c = a + (b + c)$	Associative	Same as regular algebra
$aa' = 0$ $a + a' = 1$	Complement (AND) Complement (OR)	(AND) Clearly one of a, a' must be 0: $1 \cdot 0 = 0 \cdot 1 = 0$ (OR) Clearly one of a, a' must be 1: $1 + 0 = 0 + 1 = 1$.
$a \cdot 1 = a$ $a + 0 = a$	Identity (AND) Identity (OR)	(AND) Result of $a \cdot 1$ is always a 's value: $0 \cdot 1 = 0 \quad 1 \cdot 1 = 1$. (OR) Result of $a + 0$ is always a 's value: $0 + 0 = 0 \quad 1 + 0 = 1$.
$a \cdot 0 = 0$ $a + 1 = 1$	Null elements	Result doesn't depend on the value of a .
$a \cdot a = a$ $a + a = a$	Idempotent	Duplicate values can be removed.
$(a')' = a$	Involution	$(0)' = (1)' = 0$ $(1)' = (0)' = 1$
$(ab)' = a' + b'$ $(a + b)' = a'b'$	DeMorgan's law	<i>Discussed in another section</i>

7.2 DeMorgan's Law

- DeMorgan's law, a Boolean algebra property for contemplating an expression, comes in 2 forms:

$$1. (a+b)' = a'b'$$

$$2. (ab)' = a' + b'$$

- Each literal is complemented

- the AND/ORs swap

- $y = (ab)'$ is NOT in sum-of-products form


- $y = a' + b'$ IS in sum-of-products form.

7.3 NAND / NOR (universal gates)

- A NAND gate is the opposite (the NOT, hence the "N") of an AND gate, outputting a 0 if all inputs are 1s; otherwise the output is 1.

Figure 7.3.1: NAND truth table and gate.


a	b	f
0	0	1
0	1	1
1	0	1
1	1	0

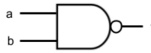

- NAND gates are universal gates.

- A universal gate is a single gate type that can implement any combinational circuit.

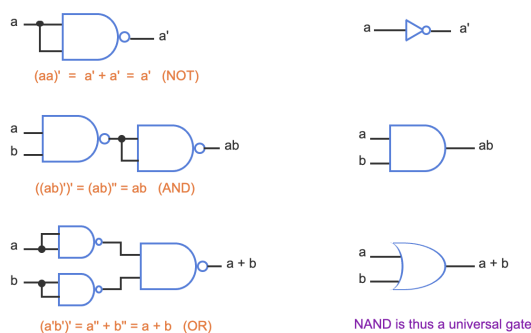↳ NAND can implement NOT, AND, and OR as shown below:




Because NAND can implement NOT, AND, and OR, any circuit can be implemented with just NANDs. NAND is thus a universal gate.


• A chip with prefabricated gates is called a gate-array ASIC. ASIC is short for application-specific integrated circuit.

• Converting to NAND gates:

 
↳ Tying together the inputs of a NAND gate is equivalent to a NOT gate.



 ↳ Inverting the output of a NAND gate is equivalent to an AND gate.



 ↳ Inverting the inputs of a NAND gate is equivalent to an OR gate.



• A NOR gate is the opposite of an OR gate, outputting 0 if any of the inputs are 1s; otherwise the output is 1.

↳ NOR is also a universal gate

Figure 7.3.2: NOR truth table and gate.

a	b	f
0	0	1
0	1	0
1	0	0
1	1	0



7.5 Sum-of-Products Form

- A product term consists of one or more variables, like $ab'c$, joined by AND.
- An expression in sum-of-products form consists of product terms joined by OR, such as $ab'c' + ab$
- Because similarities with regular algebra, convention uses the word "product" for AND and "sum" for OR; hence the name "sum-of-products"
- Converting sum-of-products to a circuit:
 - A sum-of-products equation can be easily converted to a two-level circuit, consisting of a column of AND gates (one gate per product term), followed by an OR gate (the NOT gates preceding the AND gates aren't considered a level.)
- A processor executes computer programs.
 - ↳ Devices such as keyboards or USB ports surrounding a processor may request the processor to execute a sub-program on behalf of that device, a request known as an interrupt.

7.6 Sum-of-minterms form

- A canonical form of a Boolean equation is a standard equation form for a function.
- Sum-of-minterms form is a canonical form of a Boolean equation where the right-side expression is a sum of products with each product a unique minterm.
- A minterm is a product term having exactly one literal for every function variable.
- A literal is a variable appearance, in true or complemented form, in an expression, such as b or b' .

Transforming to sum-of-minterms

- A sum-of-products equation can be transformed to sum-of-minterms form by multiplying each product term by $(v+v')$ for any missing variable v to create the minterm (removing redundant minterms)
↳ Note: $(v+v')$ is 1.

Ex Equation \rightarrow Sum-of-Minterms form

$$y = (a+c)b$$

$$y = ac + bc$$

$$y = ab(1) + bc(1)$$

$$y = ab(c+c') + bc(a+a')$$

$$y = abc + abc' + abc + a'bc$$

$$y = a'bc + abc' + abc$$

- Because sum-of-minterms form is canonical, you can put two different equations into sum-of-minterms form to see if they represent the same function.

• A compact function notation represents each minterm by a number.

↳ Given that $ab'c$ is 1 if $a/b/c$ are $1/0/1$, that minterm is represented as m_5 because 101 in binary is 5 in decimal.

Ex: $a'b'c'$ = m_2 because $a'b'c'$ is 1 when $a/b/c$ are $0/1/0$. $010_2 \rightarrow 2_{10}$

Ex: abc' = m_6 because abc' is 1 when $a/b/c$ is $1/1/0$. $110_2 \rightarrow 6_{10}$

Ex $f(a,b,c) = ab$

$$\rightarrow ab(c+c')$$

$$\rightarrow abc + abc'$$

$$\rightarrow m_7 + m_6$$

$$\rightarrow m_6 + m_7 \text{ (since minterms are usually in ascending order)}$$